

Embedded Systems

Digital-to-Analog & Analog-to-Digital Converters



Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 1


A/D and D/A Converters

- **Two basic types of converters:**
 - Digital-to-analog (DACs or D/As)
 - Analog-to-digital (ADCs or A/Ds)
- **Frequently utilized in embedded systems**
 - Often integrated into μ C (ATmega88: 10-bit ADC, but no DAC)
- **Applications include:**
 - Digital signal processing (DSP): audio, radio, ...
 - Imaging (CCD)
 - Medical applications
 - Instrumentation, data loggers, ...
 - Digital offset and gain adjustment
 - Sensors: temperature, weight bridge, ...
 - Control systems: motor, temperature, digital servos, ...
 - Communications, GPS, ...
 - ...

Slide 2

Application Example - Digital Signal Processing

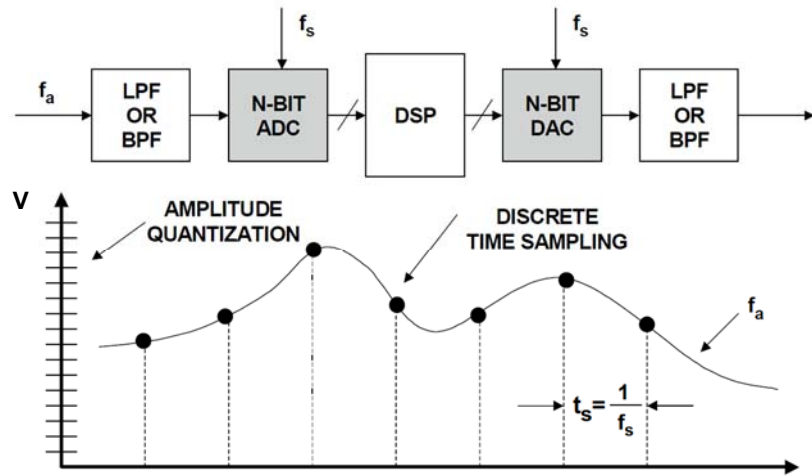- E.g., digital audio filter, software-defined radio (SDR), ...




Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 3

Converters

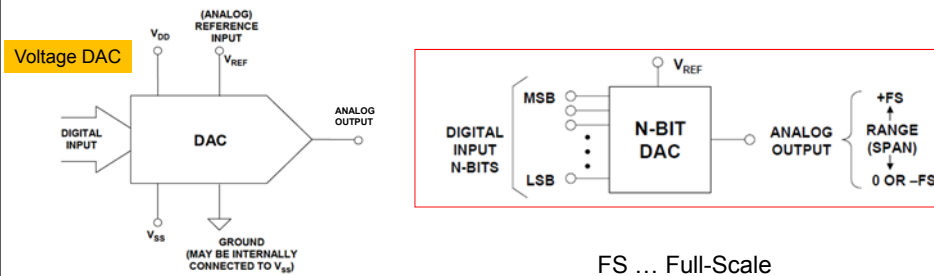- DACs** convert a digital input value to a voltage or current
 - Voltage/current is a proportion of a reference voltage/current
 - The proportion is defined by the digital input applied




FS ... Full-Scale

Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 4

Converters

 - **ADCs** convert a voltage or current to a digital output value
 - A digital representation of the analog voltage/current that is applied to the ADC input is outputted
 - The representation is proportional to a reference voltage/current



Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 5

Pre- and Post-Processing & Accuracy vs Resolution

- **ADC** → voltages and currents must be “normalized” to ranges compatible with **ADC** input ranges
 - often a preprocessing of input signals is required
- **DAC** → analog output voltages or currents from **DACs** are direct and in normalized form
 - signals often need post-processing (e.g., scaled/amplified, filtered, etc.).

Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 6

A/D and D/A Converters


- Different architectures
- It is important to select a suitable A/D or D/A converter for a given application → design requirements
 - Processing speed
 - Resolution
 - Accuracy, linearity, ...
 - Power consumption
 - ...
- **ADC architectures:**
 - successive approximation, flash, dual slope, sigma-delta, ...
- **DAC architectures:**
 - string, R-2R, PWM, ...

Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 7

Aliasing and Sampling Frequency

 - The required conversion speed depends on the application (e.g., sampling/reproducing an audio signal, thermocouples, HF transceiver, ...)
- A signal with a maximum BANDWIDTH f_a must be sampled at a rate $f_s > 2 f_a$, or information about the signal will be lost because of aliasing.



NOTE: f_a IS SLIGHTLY LESS THAN f_s


→ Oscilloscope

Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 8

Resolution of Data Converters

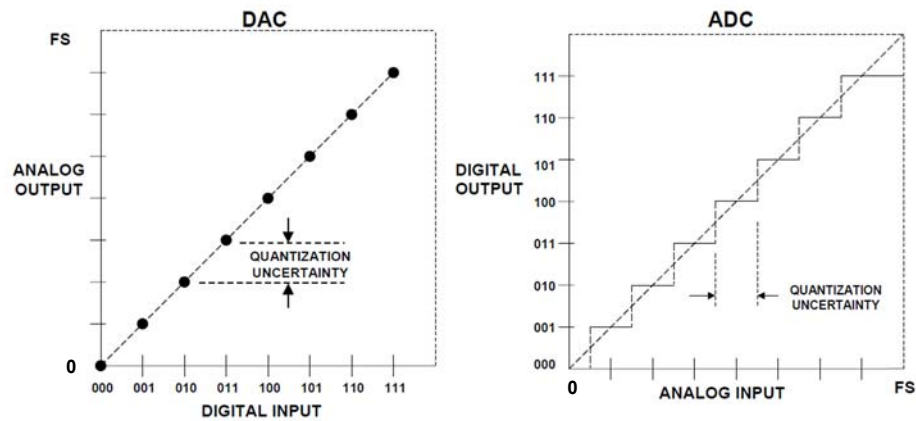- Transfer Functions for Ideal 3-Bit DAC and ADC



→ Resolution affects quantization uncertainty → signal quantization errors

Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 9

Resolution of Data Converters

- The digital input or output can have 1 to 32 bits
 - The greater the number of bits, the finer the resolution
- Example:
 - The 10-bit ADC used by the Atmega88 with a 5 V reference (FS)
 - Has $2^{10} = 1024$ possible output codes
 - Can resolve $5/2^{10} = 5/1024 = 4.88$ mV

Typically:

$$\frac{\text{Code}_{\text{Out/In}}}{2^N} = \frac{S_{\text{In/Out}}}{FS}$$

fractional binary

Code_{Out/In} ... code produced by ADC or code sent to DAC

N ... number of bits

S_{In/Out} ... input signal to ADC or output signal of DAC

FS ... full-scale (often equivalent to reference)

Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 10

Resolution of Data Converters

- The resolution of data converters may be expressed in several different ways
- Quantization: The Size of a Least Significant Bit (LSB)

RESOLUTION N	2^N	VOLTAGE (10V FS)	ppm FS	% FS	dB FS
2-bit	4	2.5 V	250,000	25	- 12
4-bit	16	625 mV	62,500	6.25	- 24
6-bit	64	156 mV	15,625	1.56	- 36
8-bit	256	39.1 mV	3,906	0.39	- 48
10-bit	1,024	9.77 mV (10 mV)	977	0.098	- 60
12-bit	4,096	2.44 mV	244	0.024	- 72
14-bit	16,384	610 μ V	61	0.0061	- 84
16-bit	65,536	153 μ V	15	0.0015	- 96
18-bit	262,144	38 μ V	4	0.0004	- 108
20-bit	1,048,576	9.54 μ V (10 μ V)	1	0.0001	- 120
22-bit	4,194,304	2.38 μ V	0.24	0.000024	- 132
24-bit	16,777,216	596 nV*	0.06	0.000006	- 144

*600nV is the Johnson Noise in a 10kHz BW of a 2.2k Ω Resistor @ 25°C

Example - D/A Converter

- An engineer needs to select a DAC that can produce an output voltage in the range of 0 to 3 V. The voltage increment ΔV needs to be ≤ 1 mV.
- Q1: How many bits (N) will be needed to meet this specification?
- Q2: What will be the value of ΔV ?

Fractional Binary Numbers

- For ADCs & DACs **fractional binary coding** is utilized, which is always normalized to full-scale (\rightarrow ref. voltage)
- Integer binary can be interpreted as fractional binary if all integer values are divided by 2^N

WHOLE NUMBERS:

$$\text{Number}_{10} = a_{N-1}2^{N-1} + a_{N-2}2^{N-2} + \dots + a_12^1 + a_02^0$$

\uparrow MSB \uparrow LSB

Example: $1011_2 = (1 \times 2^3) + (0 \times 2^2) + (1 \times 2^1) + (1 \times 2^0)$
 $= 8 + 0 + 2 + 1 = 11_{10}$

FRACTIONAL NUMBERS:

$$\text{Number}_{10} = a_{N-1}2^{-1} + a_{N-2}2^{-2} + \dots + a_12^{-(N-1)} + a_02^{-N}$$

\uparrow MSB \uparrow LSB

Example: $0.1011_2 = (1 \times 0.5) + (0 \times 0.25) + (1 \times 0.125) + (1 \times 0.0625)$
 $= 0.5 + 0 + 0.125 + 0.0625 = 0.6875_{10}$

N=4

Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 13

Unipolar Codes

- Coding method is related to the
 - analog input range of an ADC or
 - analog output range of a DAC
- The simplest case is when the input to the ADC or the output of the DAC is always a unipolar (positive) voltage/current

Example:
4-bit converter


BASE 10 NUMBER	SCALE	+10 V FS	BINARY
+15	+FS - 1 LSB = 15/16 FS	9.375	1111
+14	+7/8 FS	8.750	1110
+13	+13/16 FS	8.125	1101
+12	+3/4 FS	7.500	1100
+11	+11/16 FS	6.875	1011
+10	+5/8 FS	6.250	1010
+9	+9/16 FS	5.625	1001
+8	+1/2 FS	5.000	1000
+7	+7/16 FS	4.375	0111
+6	+3/8 FS	3.750	0110
+5	+5/16 FS	3.125	0101
+4	+1/4 FS	2.500	0100
+3	+3/16 FS	1.875	0011
+2	+1/8 FS	1.250	0010
+1	1 LSB = +1/16 FS	0.625	0001
0	0	0.000	0000

Embedded Systems, ECE:3360. The University of Iowa, 2019


Slide 14

Unipolar Codes

DAC

 


ADC

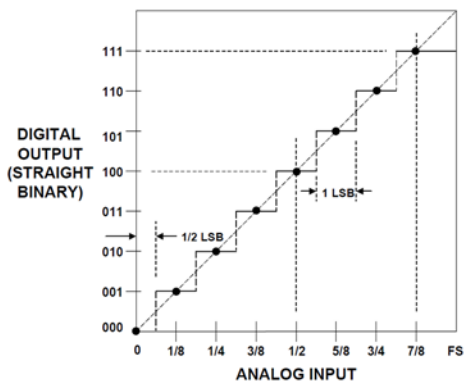

Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 15

Unipolar and Bipolar DACs

 

Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 16

Bipolar Codes

- For some applications it is desirable to represent both positive and negative analog quantities with binary codes
- Either *offset binary*, *two's complement*, *ones complement*, and *sign magnitude* codes will accomplish this, but *offset binary* and *two's complement* are by far the most popular

Example:
4-bit converter

BASE 10 NUMBER	SCALE	±5V FS	OFFSET BINARY	TWOS COMP.	ONES COMP.	SIGN MAG.
+7	+FS - 1LSB = +7/8 FS	+4.375	1 1 1 1	0 1 1 1	0 1 1 1	0 1 1 1
+6	+3/4 FS	+3.750	1 1 1 0	0 1 1 0	0 1 1 0	0 1 1 0
+5	+5/8 FS	+3.125	1 1 0 1	0 1 0 1	0 1 0 1	0 1 0 1
+4	+1/2 FS	+2.500	1 1 0 0	0 1 0 0	0 1 0 0	0 1 0 0
+3	+3/8 FS	+1.875	1 0 1 1	0 0 1 1	0 0 1 1	0 0 1 1
+2	+1/4 FS	+1.250	1 0 1 0	0 0 1 0	0 0 1 0	0 0 1 0
+1	+1/8 FS	+0.625	1 0 0 1	0 0 0 1	0 0 0 1	0 0 0 1
0	0	0.000	1 0 0 0	0 0 0 0	*0 0 0 0	*1 0 0 0
-1	-1/8 FS	-0.625	0 1 1 1	1 1 1 1	1 1 1 0	1 0 0 1
-2	-1/4 FS	-1.250	0 1 1 0	1 1 1 0	1 1 0 1	1 0 1 0
-3	-3/8 FS	-1.875	0 1 0 1	1 1 0 1	1 1 0 0	1 0 1 1
-4	-1/2 FS	-2.500	0 1 0 0	1 1 0 0	1 0 1 1	1 1 0 0
-5	-5/8 FS	-3.125	0 0 1 1	1 0 1 1	1 0 1 0	1 1 0 1
-6	-3/4 FS	-3.750	0 0 1 0	1 0 1 0	1 0 0 1	1 1 1 0
-7	-FS + 1LSB = -7/8 FS	-4.375	0 0 0 1	1 0 0 1	1 0 0 0	1 1 1 1
-8	-FS	-5.000	0 0 0 0	1 0 0 0		


CODES NOT NORMALLY USED
IN COMPUTATIONS

* 0+ 0 0 0 0 0 0 0 0
0- 1 1 1 1 1 0 0 0


Slide 17

Bipolar Codes


DAC

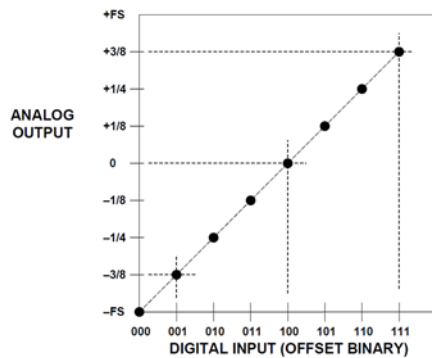

ADC

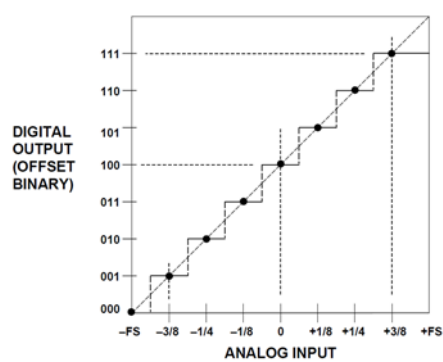

ADC - Errors

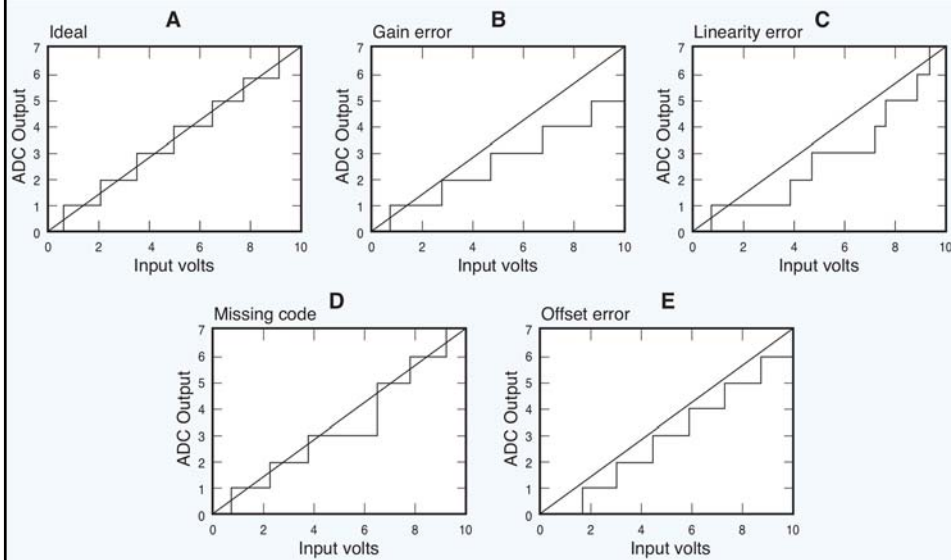


Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 19

Non-Ideal Converters

 - Transfer Functions for Non-Ideal 3-Bit DAC and ADC



Transfer Functions for Non-Ideal 3-Bit DAC and ADC

Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 20


DACs

Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 21

DACs

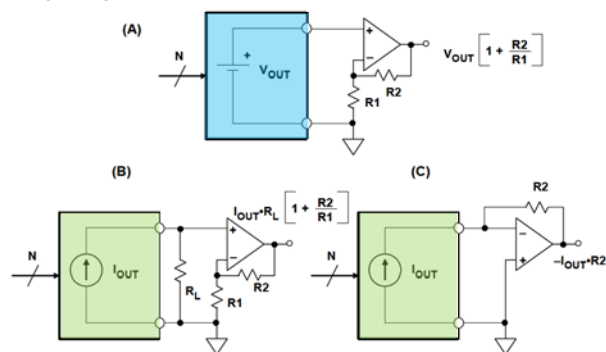- Many DACs require a voltage reference
 - Effects DAC performance (e.g., accuracy, noise, drift, ...)
- Voltage DACs may require a buffer/amplifier (A)
- Some DACs output a current
 - an op-amp can be used to perform the current-to-voltage (I/V) conversion (B, C)




Buffering DAC Outputs with Op Amps

Slide 22

Simple Voltage-Output DAC

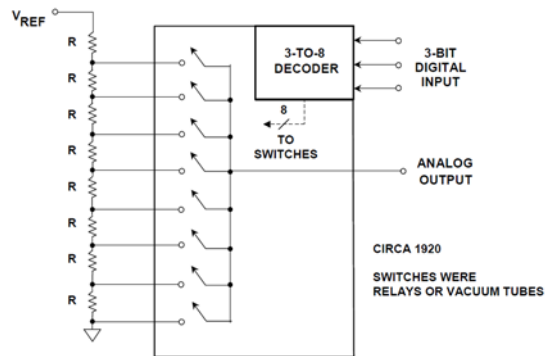- A N-bit String DAC uses 2^N resistors and 2^N (CMOS) switches → high complexity for large N
- Nonlinear versions are also possible
- Output impedance depends on input → use a voltage buffer




Simplest Voltage-Output Thermometer DAC:
The Kelvin Divider

Slide 23

Digital Potentiometers

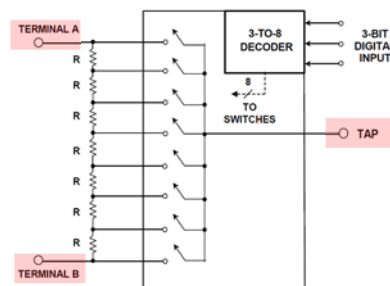- Another variation of the string DAC is the digital potentiometer
 - Better “adjustability” than their mechanical counterparts
 - Immune to mechanical vibration and oxidation of the wiper contact
 - Adjustments can be made without human intervention
 - Typically, the voltage on the input pins cannot exceed the supplies (CMOS switches)




A Slight Modification to a Kelvin DAC Yields a "Digital Potentiometer"

Slide 24

Thermometer Current-Output DAC

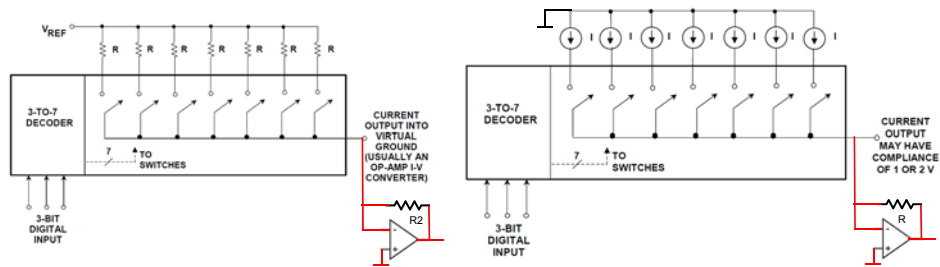- Analogous to a string DAC
- Consists of $2^N - 1$ switchable current sources (resistors and a voltage reference or active current sources) connected to an output terminal
- Output must be at or close to ground \rightarrow I-V converter



\rightarrow switching a current on and off is disruptive \rightarrow glitches


Solution: complementary current outputs

Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 25

Thermometer DAC with Complementary Current Outputs

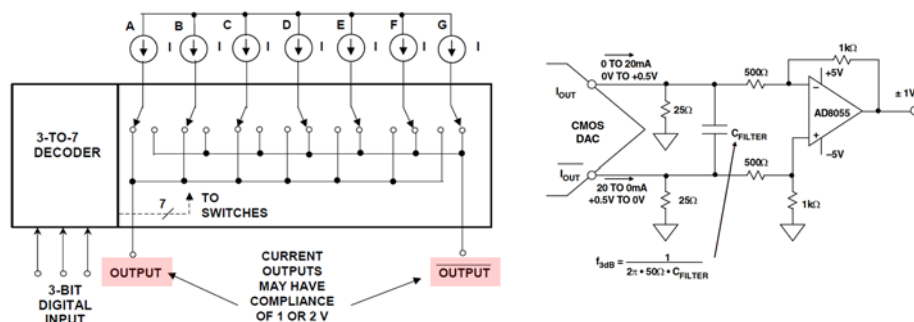- Two options for I-V conversion:
 - Connect one line to ground \rightarrow standard I-V converter
 - Differential DC-coupled I-V converter




Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 26

Current-Mode Binary-Weighted DACs

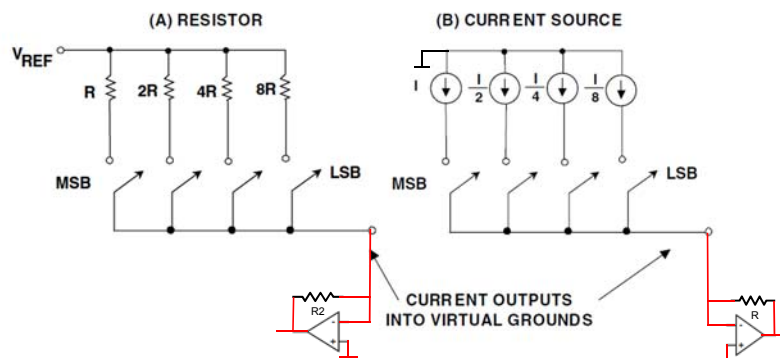- **Implementation:**
 - N weighted resistors and a voltage reference or
 - N weighted current sources with
 - ratio 1:2:4: ... : $2^{(N-1)}$




◆ DIFFICULT TO FABRICATE IN IC FORM DUE TO LARGE RESISTOR OR CURRENT RATIOS FOR HIGH RESOLUTIONS

Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 27

R-2R Resistor Ladder

 - R-2R resistor ladder → the most common DAC building-block
- It uses resistors of only two different values (ratio is 1:2)
- An N-bit DAC → 2N resistors, which are quite easy to trim




Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 28

R-2R Resistor Ladder based DAC

- R-2R resistor ladder →

- Current output

 

- Voltage output


 



Figure 15. DAC Simplified Circuit Diagram

embedded S

 

Slide 29

Example - Simple R-2R DAC (DDS)

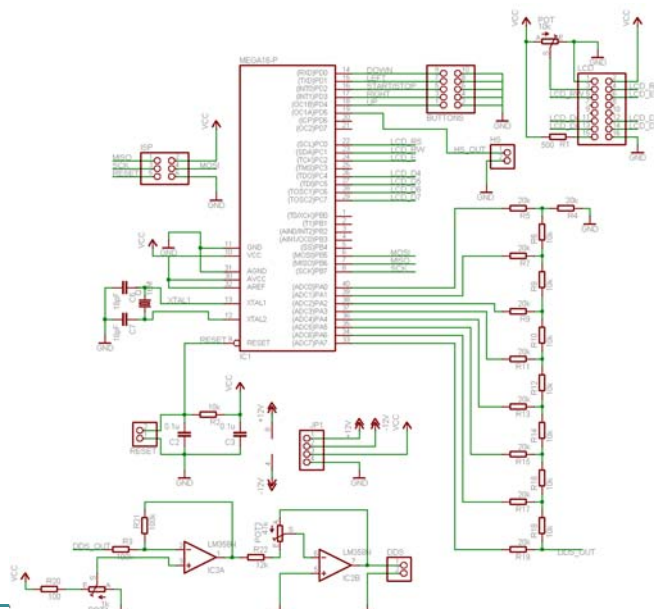


Slide 30


DAC with Pulse Width Modulation (PWM)

- PWM DAC**

 - basic idea → decomposition of a PWM signal





- Analog Filtering of PWM Signal**

 


Change of duty cycle → change of DC component

RC Low-Pass Filter

  

Output of a PWM Sine Wave

 


ADC

Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 33

The Comparator: A 1-Bit ADC

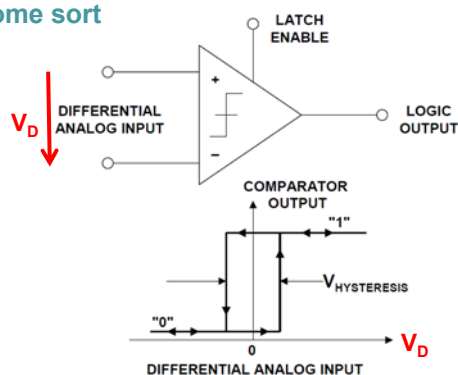- The output will be a logic "1" if $V_D > 0$ and a logic "0" for $V_D < 0$
- Some devices have a hysteresis
- → useful building block for other ADC architectures
 - → there is no ADC architecture which does not use at least one comparator of some sort




Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 34

Comparator

 - Some comparators have an internal latch
- The latch-enable signal has two states:
 - compare (track)
 - latch (hold)




Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 35

Charge Run-Down ADCs


- First samples the analog input and stores the voltage on a fixed capacitor
- The capacitor is then discharged with a constant current source → the time required for complete discharge is measured using a counter
- Accuracy depends on: C , current source, time-base, ...

 

Slide 36

Tracking ADCs

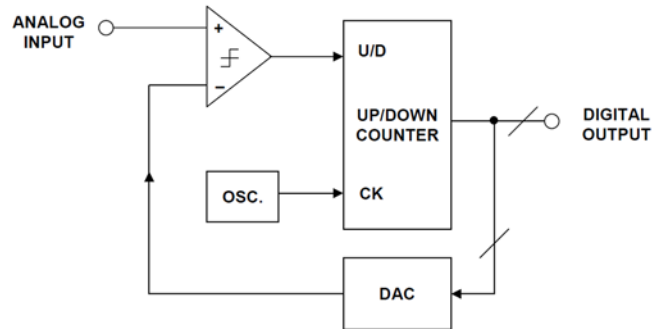- Continually compares the input signal with a reconstructed representation of the input signal (DAC)
- The up/down counter is controlled by the comparator output.
- → slow step response → not widely used




Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 37

Successive Approximation ADCs

- Used in the ATmega88PA and other μ Cs
- The mainstay of data acquisition for many years
- Recent design improvements → sampling frequency in MHz-region
- → constant conversion time for a given resolution

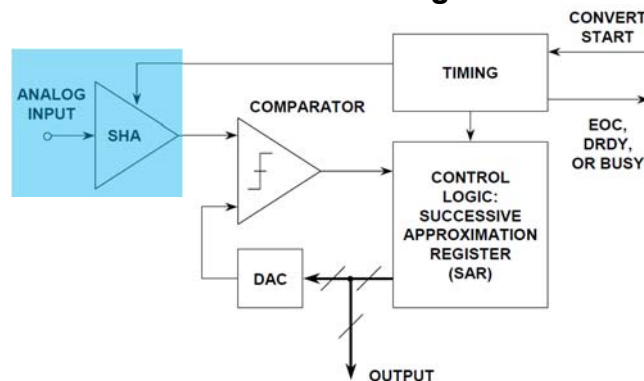

Slide 38

Successive Approximation ADCs

- Successive Approximation Algorithm (6-bit ADC)

"Balance scale" approach

MSB = 2^5



TEST

IS $X \geq 32$?




ASSUME $X = 45$

YES → RETAIN 32 → 1


Successive Approximation ADCs

 - Successive Approximation Algorithm (6-bit ADC)



TEST

IS $X \geq 32$?

 

ASSUME $X = 45$

YES → RETAIN 32 → 1

2^4




IS $X \geq (32 + 16)$?

NO → REJECT 16 → 0


Successive Approximation ADCs

 - Successive Approximation Algorithm (6-bit ADC)




Successive Approximation ADCs

 - Successive Approximation Algorithm (6-bit ADC)



Successive Approximation ADCs

 • Successive Approximation Algorithm (6-bit ADC)




Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 43

Successive Approximation ADCs

 • Successive Approximation Algorithm (6-bit ADC)




TOTALS: $X = 32 + 8 + 4 + 1 = 45_{10} = 101101_2$

Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 44

Successive Approximation ADCs

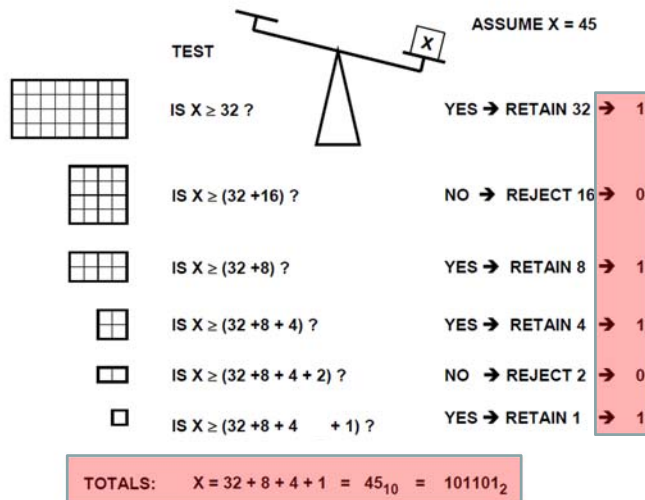- Successive Approximation Algorithm (6-bit ADC)




Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 45

Successive Approximation ADCs

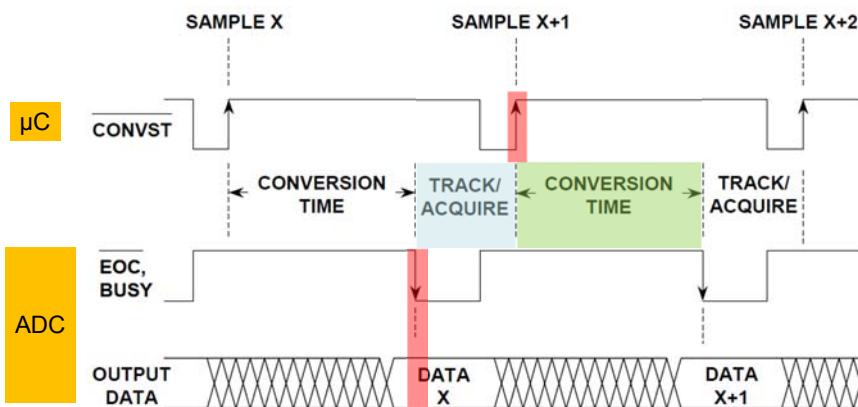- Input signal must be stable during conversion
 - Sample & hold stage
- Typical SAR ADC timing



Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 46

Successive Approximation ADCs


- Often integrated on μ Cs
 - **ATmega88:**
 - 8/10-bit SAR ADC
 - Up to 76.9 kSPS (up to 15 kSPS at max. resolution)
- Advantages
 - High Accuracy
 - Typically Low Power
 - Low cost
- Disadvantages
 - Max sample rates approximately 2-5 MHz
 - Medium resolution

Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 47

Flash Converters


- Flash (parallel) ADCs are the fastest type of ADC
- Have a large numbers of components:
 - N-bit flash ADC consists of 2^N resistors and $2^N - 1$ comparators
- Very fast, but lower resolution, high power dissipation, and expensive

 

Slide 48

Dual Slope ADCs

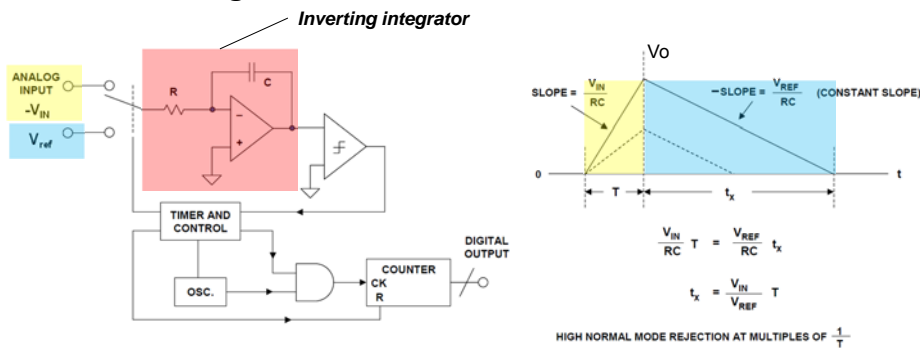- “Breakthrough” in ADCs for high resolution applications such as digital voltmeters (DVMs), etc.
- Many advantages: conversion accuracy is independent of C and clock frequency, fixed input signal integration period → noise rejection (e.g., 50/60 Hz)
- Disadvantage: slow




Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 49

Sigma-Delta (or Delta-Sigma) ADC

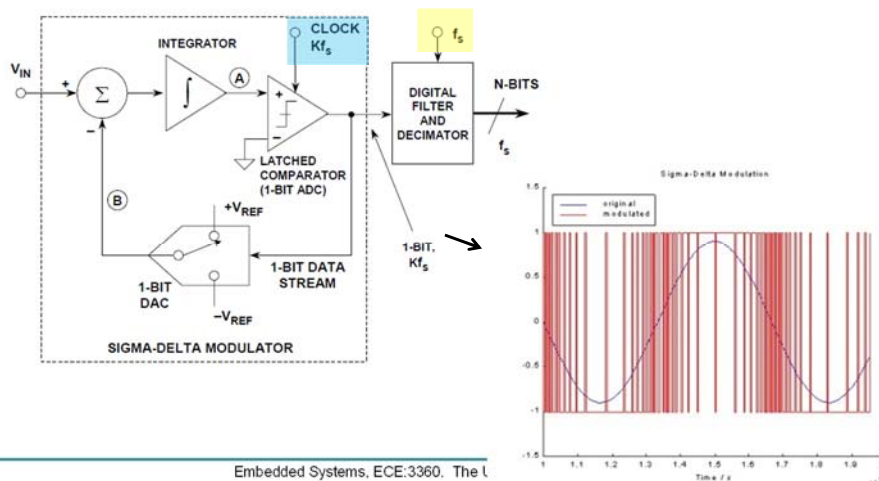
- Conversion approach: k-fold oversampling (1-bit signal) and digital filtering with down-conversion
- High resolution, high stability (averages and filters out noise), low power, moderate cost, and low to medium conversion speed



Embedded Systems, ECE:3360. The U

Voltage-to-Frequency Converter

 - A voltage-to-frequency converter (VFC) is an oscillator whose frequency is linearly proportional to a control voltage
- VFCs are typically small, cheap, and low-powered
- Can be used in combination with an optocoupler for isolation → e.g., industrial applications




- ◆ CONNECTION NEED NOT BE DIRECT
- ◆ CIRCUIT IS IDEAL FOR TELEMETRY

Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 51

Comparison of ADC Architectures

 

Embedded Systems, ECE:3360. The University of Iowa, 2019

Slide 52

... EOL